

$$V = Ri$$

$$Q = f(t)$$

$$Q = CV_C$$

$$V_C = \frac{Q}{C}$$

$$+ \mathcal{E} - V_R - V_C = 0$$

$$+ \mathcal{E} - Ri - \frac{Q}{C} = 0$$

$$\Rightarrow \mathcal{E} - R \frac{dQ}{dt} - \frac{Q}{C} = 0$$

$$\Rightarrow \mathcal{E} - \frac{Q}{C} = R \frac{dQ}{dt}$$

$$\Rightarrow \frac{\mathcal{E}C - Q}{R} = \frac{dQ}{dt}$$

$$\Rightarrow \frac{dt}{RC} = \frac{dQ}{\mathcal{E}C - Q}$$

$$\Rightarrow \int_0^t \frac{dt}{RC} = \int_{Q=0}^Q \frac{dQ}{\zeta C - Q}$$

$$\Rightarrow \frac{t}{RC} = \left[ -\ln(\zeta C - Q) \right]_{Q=0}^Q$$

$$\begin{array}{l|l} \Rightarrow \frac{t}{RC} = -\ln(\zeta C - Q) - (-\ln(\zeta C)) & \zeta C - Q = u \\ \Rightarrow \frac{t}{RC} = -(\ln(\zeta C - Q) - \ln(\zeta C)) & \Rightarrow -dQ = du \\ \Rightarrow \frac{t}{RC} = \ln\left(\frac{\zeta C - Q}{\zeta C}\right) & \int \frac{-du}{u} = -\ln u \\ & = \ln(\zeta C - Q) \end{array}$$

$$\Rightarrow e^{-t/RC} = \frac{\zeta C - Q}{\zeta C} \quad \left[ \ln A - \ln B = \ln\left(\frac{A}{B}\right) \right]$$

$$\Rightarrow \zeta C e^{-t/RC} = \zeta C - Q$$

$$\Rightarrow Q = \zeta C - \zeta C e^{-t/RC}$$

$$\therefore Q = \zeta C (1 - e^{-t/RC})$$

$$t = 0 ; \quad Q = \zeta C (1 - e^0) = \zeta C (1 - 1) = 0$$

$$t = \infty ; \quad Q = \zeta C (1 - e^{-\infty}) = \zeta C (1 - 0) = \zeta C$$

$$t = RC \boxed{T_c},$$

$$\begin{aligned} Q &= \mathcal{E}C(1 - e^{-RC/RC}) \\ &= \mathcal{E}C(1 - e^{-1}) \\ &= \mathcal{E}C\left(1 - \frac{1}{e}\right) \\ &= 0.632C \end{aligned}$$

$$V = Ri$$

$$R = \frac{V}{I}$$

$$Q = eV$$

$$C = \frac{Q}{V}$$


$$RC = \frac{V}{I} \cdot \frac{Q}{V}$$

$$= \frac{Q}{I}$$

$$= \frac{Q}{\left(\frac{Q}{T}\right)}$$

$$= Q \times \frac{T}{Q}$$

$$= T$$

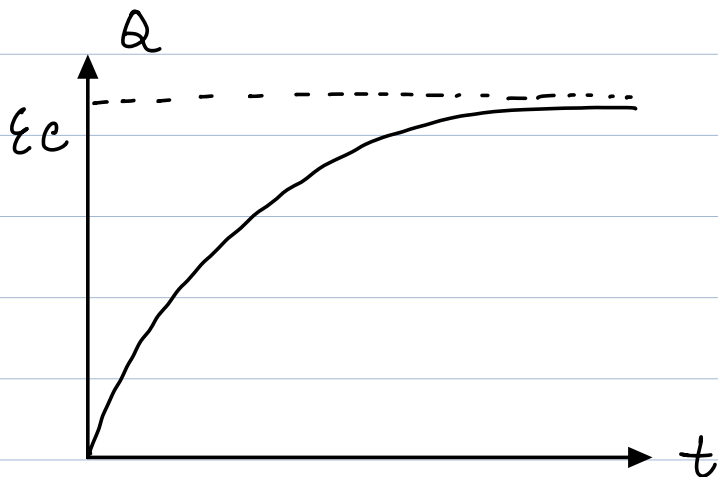

$$i = \frac{dq}{dt}$$

$$= \frac{\xi c}{RC} e^{-t/RC}$$

$$= \frac{\xi}{R} e^{-t/RC}$$


$$= i_0 e^{-t/RC}$$


$$t=0, \quad i = i_0 e^0 = i_0$$

$$t=\infty, \quad i = i_0 e^{-\infty} = \frac{i_0}{e^\infty} = 0$$

$$t=RC, \quad i = i_0 e^{-\frac{RC}{RC}}$$

$$= \frac{i_0}{e} = 0.37 i_0$$

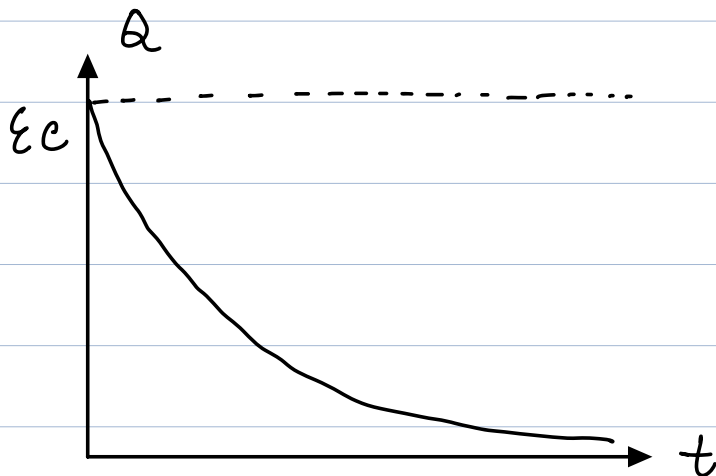

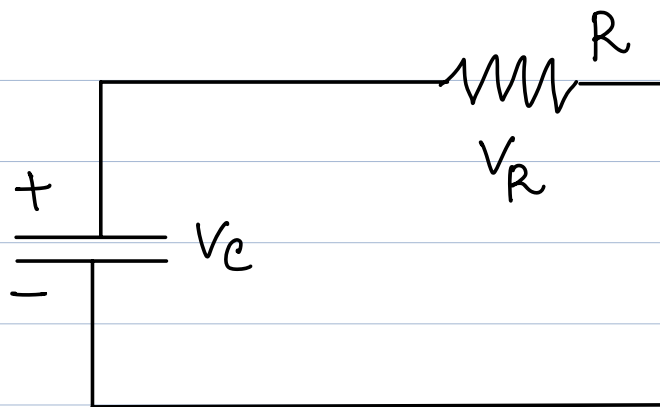

$$V_C - V_R = 0$$

$$Q = C V_C$$

$$V_C = \frac{Q}{C}$$

$$\Rightarrow \frac{Q}{C} - iR = 0$$

$$\Rightarrow \frac{Q}{C} - \left( - \frac{dQ}{dt} \right) R = 0$$

$$\Rightarrow \frac{Q}{C} + \frac{dQ}{dt} R = 0$$

$$\Rightarrow \frac{dQ}{dt} = \frac{-Q}{RC}$$

$$\Rightarrow \frac{dQ}{Q} = \frac{-dt}{RC}$$

$$\Rightarrow \int_{Q_C}^Q \frac{dQ}{Q} = - \int_{t=0}^t \frac{dt}{RC}$$

$$\Rightarrow \ln Q \Big|_{\epsilon c}^Q = \frac{-t}{RC} \Big|_0^t$$

$$\Rightarrow \ln Q - \ln(\epsilon c) = \frac{-t}{RC}$$

$$\Rightarrow \ln \frac{Q}{\epsilon c} = \frac{-t}{RC}$$

$$N = N_0 e^{-\lambda t}$$

$$\Rightarrow \frac{Q}{\epsilon c} = e^{-t/RC}$$

$$\therefore Q = \epsilon c e^{-t/RC}$$

$Q \rightarrow$  how much charge there is in the capacitor


$(\epsilon c - Q) \rightarrow$  how much charge was discharge

$$t=0, Q = \epsilon c$$


$$t = \infty, Q = 0$$

$$t = RC, Q = \epsilon c e^{-1} \\ = \epsilon \frac{c}{e}$$

$$= 0.37 \, \mathcal{E}C$$

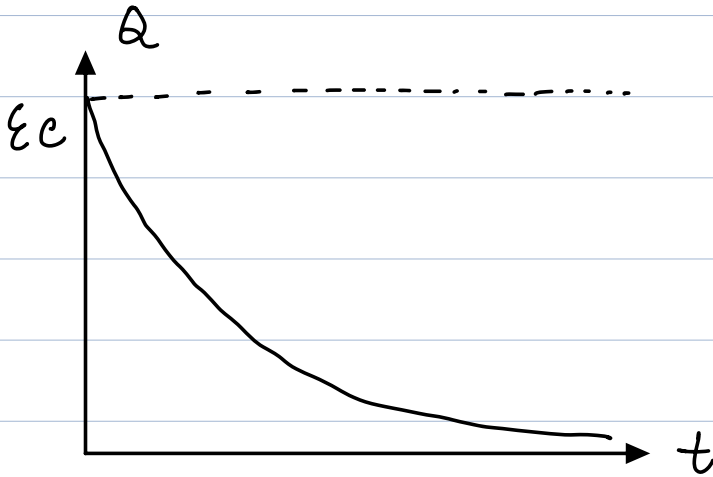
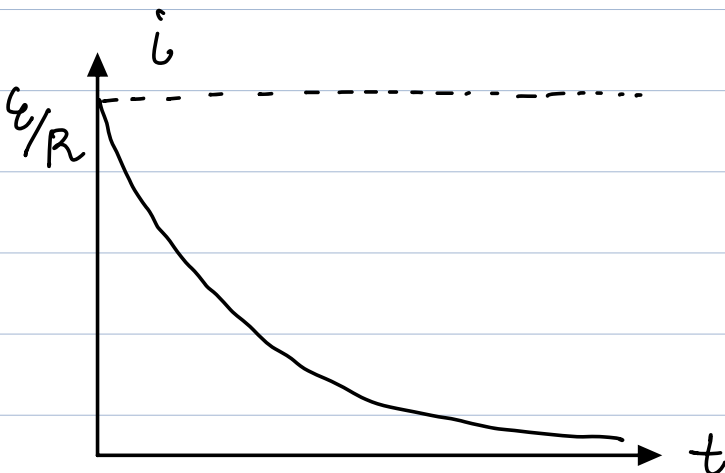
$$\begin{aligned} i &= - \frac{dQ}{dt} = - \frac{d}{dt} (\mathcal{E}C e^{-t/RC}) \\ &= -\mathcal{E}C \times \left( -\frac{1}{RC} e^{-t/RC} \right) \\ &= \frac{\mathcal{E}}{R} e^{-t/RC} \\ &= i_0 e^{-t/RC} \end{aligned}$$



$$t=0, i = \frac{\mathcal{E}}{R} = i_0$$

$$t = \infty, i = 0$$

$$t = RC, i = \frac{\mathcal{E}}{R} \cdot \frac{1}{e}$$

## Chapter-27

57, 58, 59, 61, 64, 66

$$57| \quad Q = \mathcal{E}C(1 - e^{-t/RC})$$

$$\Rightarrow CV_C = \mathcal{E}C(1 - e^{-t/RC})$$

$$\Rightarrow V_C = \mathcal{E}(1 - e^{-t/RC})$$

$$\begin{aligned} V_R &= Ri \\ &= R \frac{\mathcal{E}}{R} e^{-t/RC} \end{aligned}$$

$$\begin{aligned} V_R &= V_C \\ \Rightarrow \mathcal{E} e^{-t/RC} &= \\ &\mathcal{E}(1 - e^{-t/RC}) \end{aligned}$$

$$\Rightarrow t =$$



581

a)  $\tau = RC$

b)  $Q = \xi C$

c)  $Q = \xi C (1 - e^{-t/RC})$

$t =$

591

$$Q = \xi C (1 - e^{-t/RC})$$

$$\Rightarrow \xi C \times 0.99 = \xi C \times (1 - e^{-t/RC})$$

$$t = \underbrace{4.6 RC}$$

611

a)  $Q = \xi C (1 - e^{-t/RC})$

$$\Rightarrow CV_0 = \xi C (1 - e^{-t/RC})$$

$$\Rightarrow V_0 = \xi (1 - e^{-t/RC})$$

$$\Rightarrow 5 = 12 \left( 1 - e^{\frac{-1.3 \times 10^{-6}}{\tau}} \right)$$

$$\tau =$$

$$b) \quad \tau = RC$$

$$\Rightarrow \frac{\tau}{R} = C$$